

**Experiment – 4**

**Answer all the Questions in brief with some appropriate examples.**

- 1) Define a Switch. What is the need of a switch in an electronic circuit?
- 2) What are the different types of switches used in an electronic circuit?
- 3) What do you mean by POLE and THROW in a switch?
- 4) What is a relay? What is the function of a relay in an electronic circuit?
- 5) What is the difference between toggle switch and push button switch/Tactile Switch?
- 6) Why are there 4 pins in push button/Tactile switch?
- 7) What are the two types of push button switch?
- 8) Why are push buttons used instead of switches?
- 9) What is the difference between pull-up and pull down?
- 10) What is the difference between pull-up and pull-down resistor?
- 11) Why are pull up resistors more common than pull down resistors?
- 12) How do I choose a pull-up resistor? What should be the suitable resistance value for Pull-Up?